

CHRYSLER VOYAGER (02-05) Amplifier turn on



The relay above needs to be turned on to activate the cars amplifier.

Run a wire out to the fuse box.

1-Use the new car radio's amplifier turn on wire (blue white) to switch on this relay